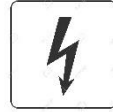


Power and Circuits




Remember that Power is the **rate** at which *energy* is used or produced

$$\text{Power} = \frac{\text{Energy}}{\text{time}}$$

$$\frac{\text{Joules}}{\text{Seconds}}$$

Watts

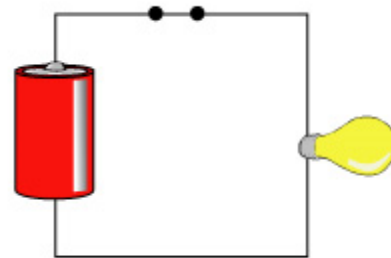Power is an important value while studying circuits because we often want to know the rate at which energy is being used by an element in a circuit or how much energy is being produced by the power source.



How does Power relate to *current*, *voltage* and *resistance*?

$$\text{Power} = I V = \frac{\text{Charge}}{\text{time}} \times \frac{\text{Energy}}{\text{Charge}} = \frac{\text{Energy}}{\text{time}} \left(\frac{\text{Joules}}{\text{Seconds}} \right) \text{ Watts}$$

Combine $P = I V$ with $V = IR$ (Ohms Law) and we get:

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

ELECTRIC POWER

Comprehension Questions:

1. What are the units for power *in terms of* Joules?
2. What is the common unit for power that is equivalent to J/s?
3. If a toaster has 3 amps running through it and a resistance of 2 ohms, what is the power it is using?
4. The voltage used by a ipod is 0.023 Volts, if it has a resistance of 0.1 ohms, determine the power it needs to operate.
5. Combine $P = I V$ with $V = IR$ (Ohms Law) to prove that $P = I^2 R$ and $P = \frac{V^2}{R}$